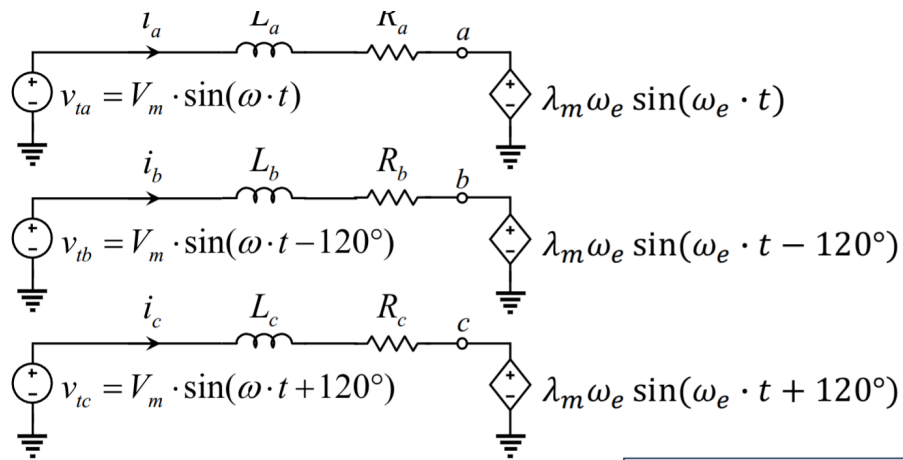


Motor Drive


Synchronous Motor Drive



- Voltage source from motor drive (power electronics)
- L_a and R_a from stator
- Dependent voltage source due to back EMF
 - function of rotating speed and flux

-
- Mechanical model/circuit for torque
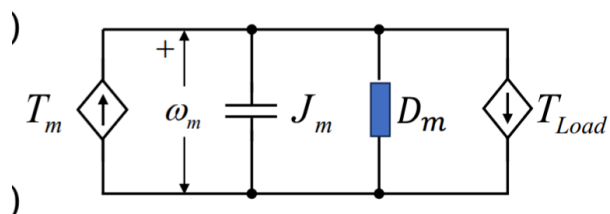
$$T_m = J_m \frac{d\omega_m}{dt} + D_m \omega_m + T_{load}$$



, Drive model on final exam